

## 5.6 IC 723 – GENERAL PURPOSE REGULATOR


Disadvantages of fixed voltage regulator:

1. Do not have the shot circuit
2. Output voltage is not adjustable

These limitations can be overcomes in IC723.

Features of IC723:

1. Unregulated dc supply voltage at the input between 9.5V & 40V
2. Adjustable regulated output voltage between 2 to 3V.
3. Maximum load current of 150 mA ( $I_{Lmax} = 150mA$ ).
4. With the additional transistor used,  $I_{Lmax}$  upto 10A is obtainable.
5. Positive or Negative supply operation
6. Internal Power dissipation of 800mW.
7. Built in short circuit protection.
8. Very low temperature drift.
9. High ripple rejection.

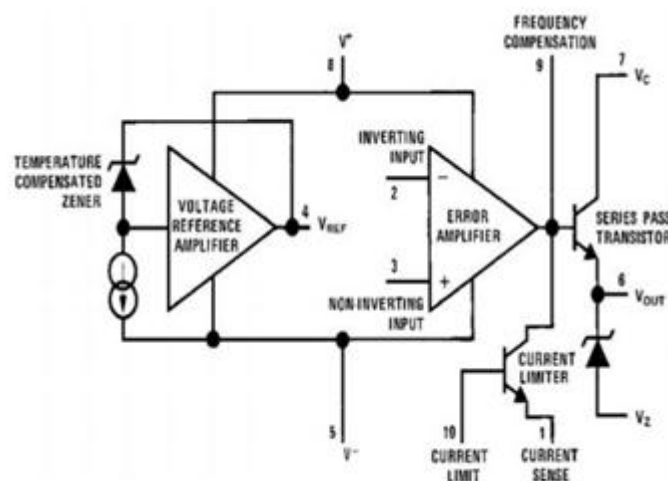

**Figure 5.6.1 Functional block diagram of IC723**

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

Functional block diagram of IC723 is shown in figure 5.6.1. The simplified functional block diagram can be divided into 4 blocks.

#### 1. Reference Generating block:

The temperature compensated Zener diode, constant current source & voltage reference amplifier together form the reference generating block. The Zener diode is used to generate a fixed reference voltage internally. Constant current source will make the Zener diode to operate at a fixed point & it is applied to the Non – inverting terminal of error amplifier. The Unregulated input voltage  $\pm V_{cc}$  is applied to the voltage reference amplifier as well as error amplifier.

#### 2. Error Amplifier:

Error amplifier is a high gain differential amplifier with 2 input (inverting & Non-inverting). The Non-inverting terminal is connected to the internally generated reference voltage. The Inverting terminal is connected to the full regulated output voltage.

#### 3. Series Pass Transistor:

Q1 is the internal series pass transistor which is driven by the error amplifier. This transistor actually acts as a variable resistor & regulates the output voltage. The collector of transistor Q1 is connected to the Un-regulated power supply. The maximum collector voltage of Q1 is limited to 36Volts. The maximum current which can be supplied by Q1 is 150mA.

#### 4. Circuitry to limit the current:

The internal transistor Q2 is used for current sensing & limiting. Q2 is normally OFF transistor. It turns ON when the  $I_L$  exceeds a predetermined limit. Low voltage, Low current is capable of supplying load voltage which is equal to or between 2 to 7Volts. Pin diagram of IC723 in figure 5.6.2.


$$V_{load} = 2 \text{ to } 7V \text{ and } I_{load} = 50mA$$

NC	1	14	NC	
Current limit	2	13	Frequency compensation	
Current sense	3	12	+V <sub>CC</sub>	
Inverting Input	4	IC 723	11	V <sub>C</sub>
Non-Inverting Input	5		10	V <sub>O</sub>
V <sub>ref</sub>	6		9	V <sub>Z</sub>
-V <sub>CC</sub>	7		8	NC

**Figure 5.6.2. Pin diagram of IC723**

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

### IC723 as a LOW voltage LOW current:

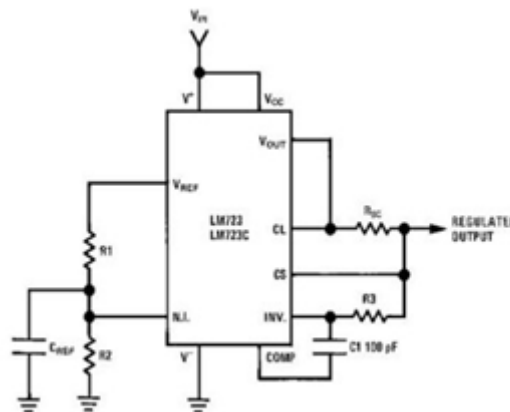

**Figure 5.6.3. Typical circuit connection diagram**

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

- Circuit connection is shown in fig 3.  $R_1$  &  $R_2$  form a potential divider between  $V_{ref}$  & Gnd.
- The Voltage across  $R_2$  is connected to the Non – inverting terminal of the regulator

$$I_C V_{non-inv} = R_2 / (R_1 + R_2) V_{ref}$$

- Gain of the internal error amplifier is large

$$V_{non-inv} = V_{in}$$

- Therefore the  $V_O$  is connected to the Inverting terminal through  $R_3$  &  $R_{SC}$  must also

be equal to  $V_{\text{non-inv}}$

$$V_o = V_{\text{non-inv}} = \frac{R_2}{(R_1+R_2)} V_{\text{ref}}$$

$R_1$  &  $R_2$  can be in the range of 1 K $\Omega$  to 10K $\Omega$  & value of  $R_3$  is given by

$$R_3 = R_1 \parallel R_2 = \frac{R_1 R_2}{(R_1+R_2)}$$

$R_{sc}$  (current sensing resistor) is connected between  $C_s$  &  $CL$ . The voltage drop across  $R_{sc}$  is proportional to the  $I_L$ .

- This resistor supplies the output voltage in the range of 2 to 7 volts, but the load current can be higher than 150mA.
- The current sourcing capacity is increased by including a transistor Q in the circuit.
- The output voltage,  $V_o = \frac{R_2}{(R_1+R_2)} V_{\text{ref}}$

### IC723 as a HIGH voltage LOW Current:

- This circuit is capable of supplying a regulated output voltage between the ranges of 7 to 37 volts with a maximum load current of 150 mA.
- The Non – inverting terminal is now connected to  $V_{\text{ref}}$  through resistance  $R_3$ .
- The value of  $R_1$  &  $R_2$  is adjusted in order to get a voltage of  $V_{\text{ref}}$  at the inverting terminal at the desired output.

$$V_{\text{in}} = V_{\text{ref}} = \frac{R_2}{(R_1+R_2)} V_o$$


$$V_o = [1+R_1/R_2] V_{\text{in}}$$

- $R_{sc}$  is connected between  $CL$  &  $C_s$  terminals as before & it provides the shortCircuit current limiting  $R_{sc} = 0.6/I_{\text{limit}}$
- The value of resistors  $R_3$  is given by ,

$$R_3 = R_1 \parallel R_2 = \frac{R_1 R_2}{(R_1+R_2)}$$

**IC723 as a HIGH voltage HIGH Current:**

- An external transistor Q is added in the circuit for high voltage low current regulator to improve its current sourcing capacity. Circuit connection of IC 723 as a High voltage High current regulator is shown in figure 5.6.4. below

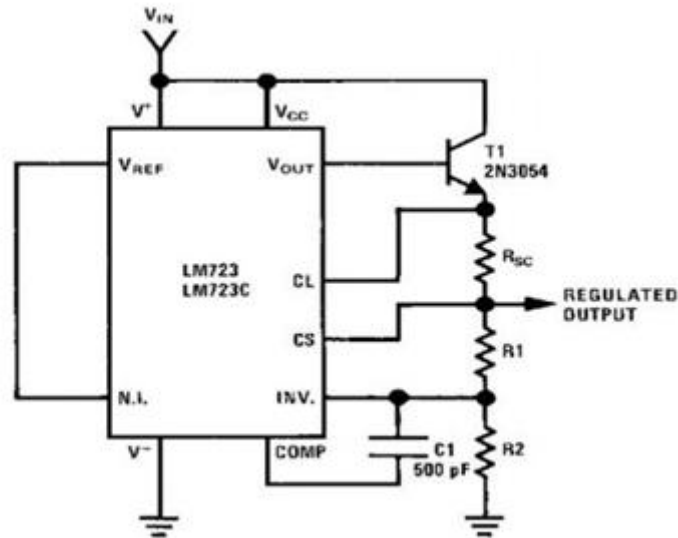

**Figure 5.6.4. Circuit connection of IC 723 as a High voltage High current regulator**

[source: [https://www.brainkart.com/subject/Linear-Integrated-Circuits\\_220/](https://www.brainkart.com/subject/Linear-Integrated-Circuits_220/)]

- For this circuit the output voltage varies between 7 & 37V.
- Transistor Q increase the current sourcing capacity thus  $I_L$  (MAX) is greater than 150mA.
- The output voltage  $V_o$  is given by ,

$$V_o = V_o = [1 + R_1/R_2] V_{in}$$

$$R_{sc} = 0.6/I \text{ limit}$$